

# University of Information Technology & Sciences (UITS)

## Department of CE

CT-1

Course: Fundamentals of Electrical Engineering (EEE 0713241)


Marks: 20

Autumn- 2024

Date: 4/9/2024

Time: 30 minutes

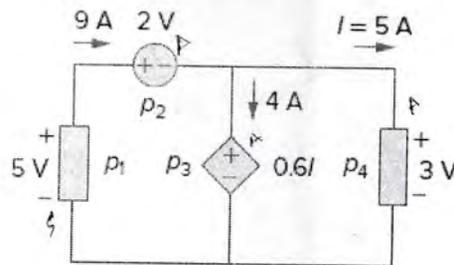1. Find the power delivered to an element at  $t = 5$  ms if the current entering its positive terminal is  $i = 5 \cos 60\pi t$  A and the voltage is  $v = (10 + 5 \int_0^t i dt)$  V. [10]
2. Compute the power absorbed or supplied by each component of the circuit in following Figure. [10]



1

*Handwritten notes:*  
 $\frac{9A}{2}$   
 $\frac{5A}{2}$   
 $\frac{2}{2}$

FEE CT 1 - CE

## OOP CT 1

University of Information Technology & Sciences (UITS)  
 Department of Computer Science and Engineering  
 Class Test-1, Course Title: Object oriented programming language  
 Course Code: CSE 0613121

1. Describe How is Java platform independent language? 2
2. Differentiate between Procedural Programming language and Object-oriented programming language 3
3. Write a java program to manage student information for a school. Follow the steps below to implement the solution. 5
  - i) Define a class **Student** with the following attributes:
    - o name (String)
    - o age (int)
    - o grade (String)
  - ii) Create a parameterized method that initializes the student's name, age, and grade.
  - iii) Implement a method called **displayInfo()** that prints the student's details in a readable format.
  - iv) In the main() method of the program:
    - Create two Student objects representing two different students.
    - Use the **displayInfo()** method to display the details of each student

# FEE CT 1

## University of Information Technology & Sciences (UITS) Department of CSE

CT-1

Course: Fundamental of Electrical Engineering (EEE 0713121)


Marks: 20

Autumn- 2024

Date: 8/9/2024

Time: 30 minutes

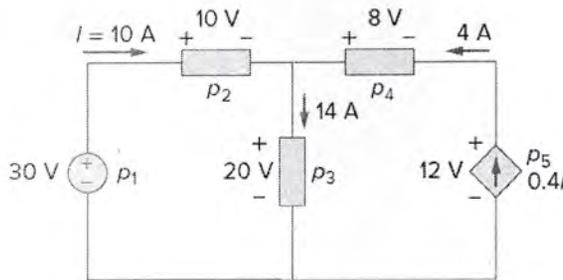- The charge entering the positive terminal of an element is  $q = 5 \sin 4\pi t$  mC. The voltage across the element (plus to minus) is  $v = 3 \cos 4\pi t$  V. Find the power delivered to the element at  $t = 0.3$  s. [10]
- Find the power absorbed by each of the elements in the following Figure. [10]



## FEE CT 1 - CE

## University of Information Technology & Sciences (UITS) Department of CE

CT-1

Course: Fundamentals of Electrical Engineering (EEE 0713241)


Marks: 20

Autumn- 2024

Date: 4/9/2024

Time: 30 minutes

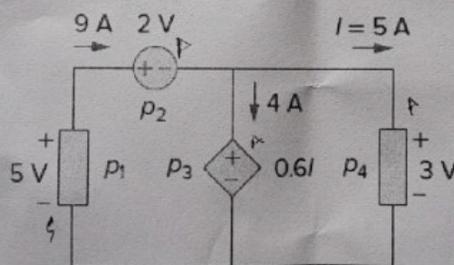- Find the power delivered to an element at  $t = 5$  ms if the current entering its positive terminal is  $i = 5 \cos 60\pi t$  A and the voltage is  $v = (10 + 5 \int_0^t i dt)$  V. [10]
- Compute the power absorbed or supplied by each component of the circuit in following Figure. [10]



Handwritten notes:  $\frac{1.9W}{2}$ ,  $\frac{5W}{2}$ ,  $\frac{10}{2}$

# FEE CT 3

## University of Information Technology & Sciences (UITS) Department of CSE

CT-3

Course: Fundamental of Electrical Engineering (EEE0713121)

Marks: 10

Autumn-2024

Date: 20/11/2024

Time: 25 minutes

1. Use mesh analysis to find the current  $i_o$  in the circuit of Figure 1.

[6]

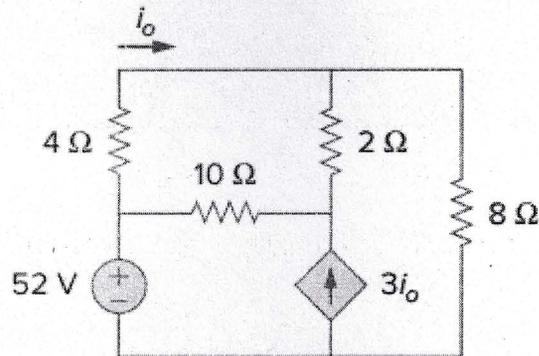


Figure 1

2. For the circuit in Figure 2, obtain  $v_1$  and  $v_2$  using nodal analysis.

[4]

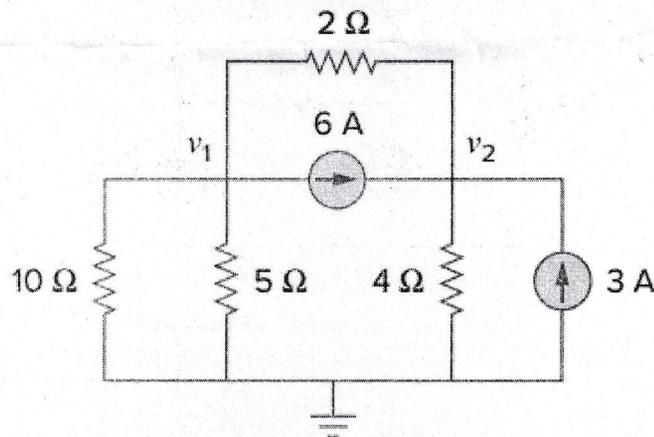


Figure 2