

University of Information Technology & Sciences (UITS)

Department of CSE

CT-1

Course: Fundamental of Electrical Engineering (EEE 0713121)

Marks: 10

Autumn- 2025

Date: 14/8/2025

Time: 20 minutes

1. Calculate the power absorbed or supply by each of the elements in the following Figure. [10]

