

University of Information Technology & Sciences (UTS)

Faculty of Science and Engineering

Department of Computer Science and Engineering

Program: B.Sc. in CSE

Term Final Question, Autumn-2023

Course Title: Fundamentals of Electrical Engineering

Course Code: EEE 151

Marks: 50

Time: 3(three) hours

(Answer all questions)

Q. No.

Marks

1. ~~30~~ For the circuit of figure 1, find R_L for maximum power delivered to R_L and determine that maximum power. [05]

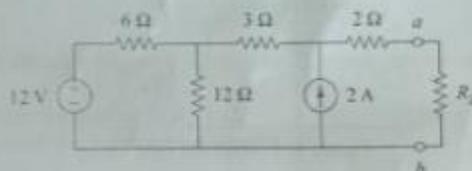


Figure 1: Circuit for 1 (a)

- b) Find the voltages at the three nonreference nodes in the circuit of figure 2. [05]

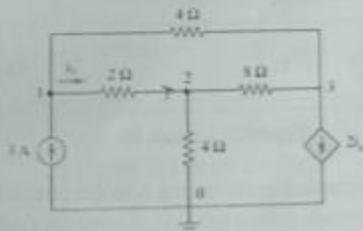


Figure 2: Circuit for 1(b)

2. a) For the circuit in figure 3, determine v and i .

[05]

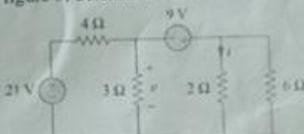


Figure 3: Circuit for 2(a)

- b) Solve for the mesh currents in figure 4.

[05]

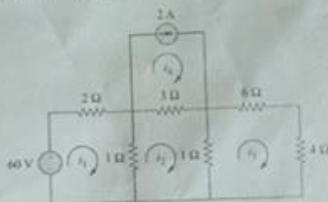


Figure 4: Circuit for 2(b)

3. a) Determine v_o in the circuit of figure 5, using the superposition principle.

[05]

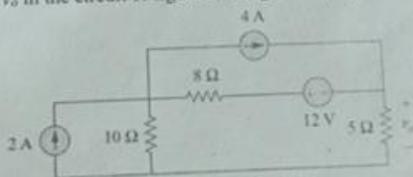


Figure 5: Circuit for 3(a)

- b) Use source transformation to determine i_o in the circuit of figure 6.

[05]

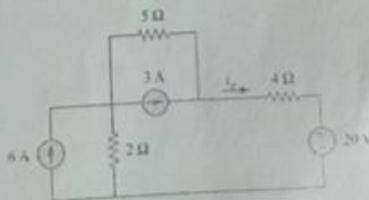


Figure 6: Circuit for 3(b)

4. a) Using Thevenin's theorem, find the equivalent circuit to the left of the terminals $a-b$ in the circuit of figure 7. And find i

[05]

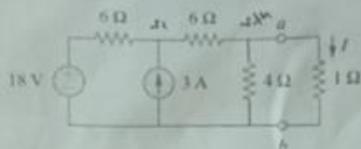


Figure 7: Circuit for 4(a)

- 4) Find the Norton equivalent circuit of the circuit in figure 8, at terminals $a-b$. [05]

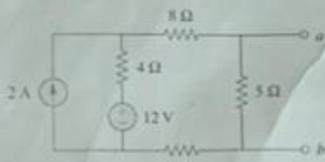


Figure 8: Circuit for 4(b)

5. i) For the circuit of figure 9, obtain the Thevenin equivalent at terminals $a-b$. [06]
 ii) Calculate the current in $R_L = 8\Omega$.
 iii) Determine the maximum power.

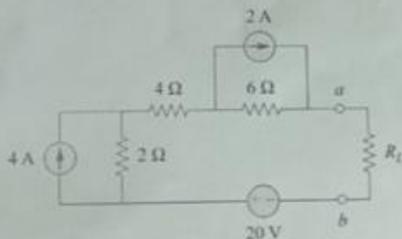


Figure 9: Circuit for 5(a)

- 6) Determine the mesh currents i_1 , i_2 in the circuit shown in figure 10. [04]

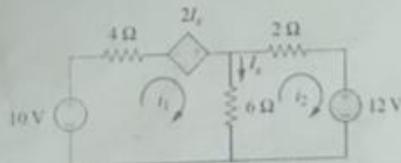


Figure 10: Circuit for 5(b)