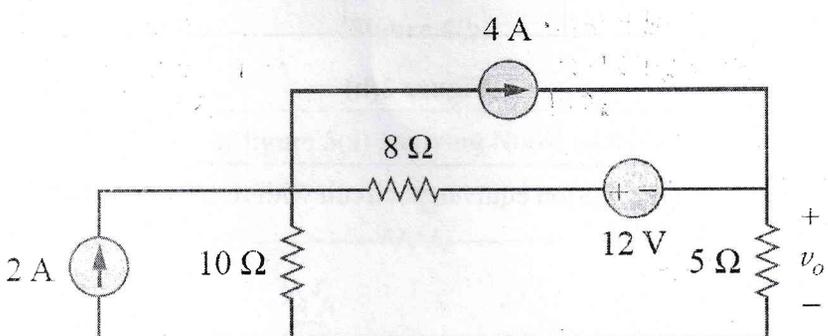
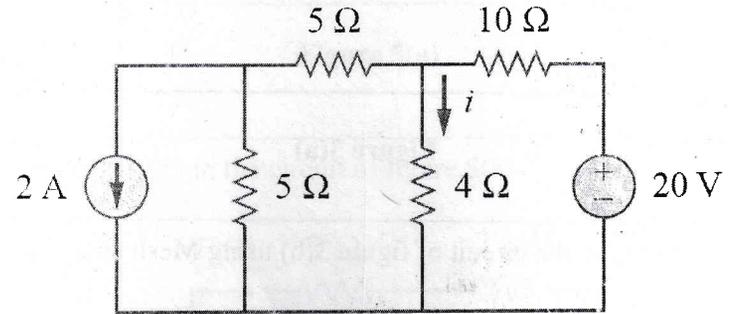


University of Information Technology & Sciences (UITS)
Faculty of Science and Engineering
Department of Computer Science and Engineering
Program: B.Sc. in CSE
Term Final Examination, Spring 2025
Course Title: Fundamental of Electrical Engineering
Course Code: EEE 0713121

Marks: 50

Time: 3(Three) hours

(Answer all questions)

Q. No.	Questions	Marks
1.	<p>a) State Superposition theorem. Calculate v_o in the circuit of figure 1(a) applying Superposition principle.</p> <div style="text-align: center;">  <p>Figure 1(a)</p> </div>	[05]
	<p>b) Use Source Transformation to calculate i in the circuit of figure 1(b).</p> <div style="text-align: center;">  <p>Figure 1(b)</p> </div>	[05]
2.	<p>a) Compute the phase angle between the following sinusoids and state which one lags the other.</p> $v_1 = 20 \sin (50t + 60^\circ)$ $v_2 = -60 \cos (50t + 100^\circ)$	[04]

- b) State Thevenin's theorem. Apply Thevenin's theorem to compute V_o in the circuit of figure 2(b). [06]

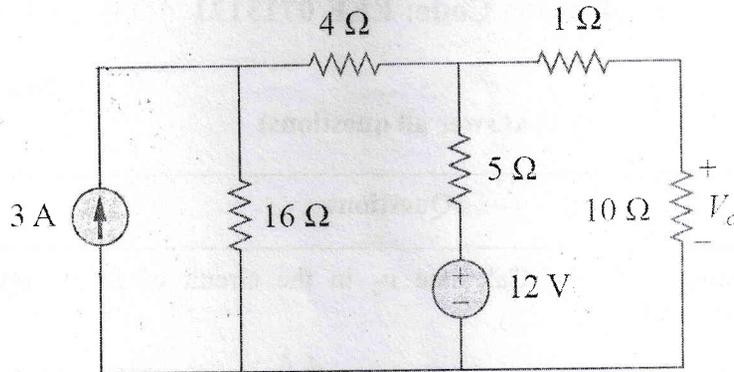


Figure 2(b)

3. a) Analyze and illustrate the Norton equivalent circuit with respect to terminals a-b in the circuit shown in figure 3(a). [05]

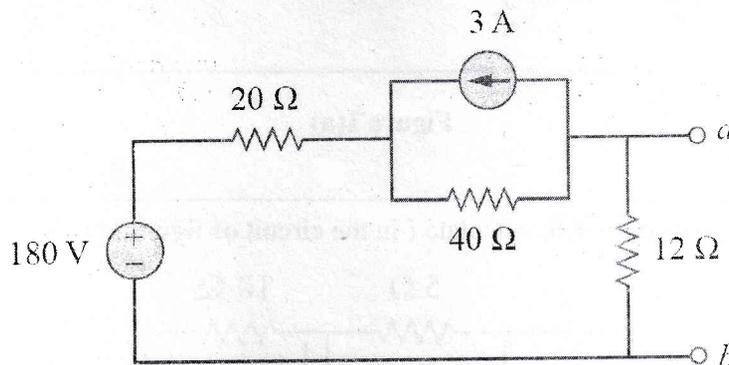


Figure 3(a)

- b) Solve for i_1 , i_2 and i_3 in the circuit of figure 3(b) using Mesh analysis. [05]

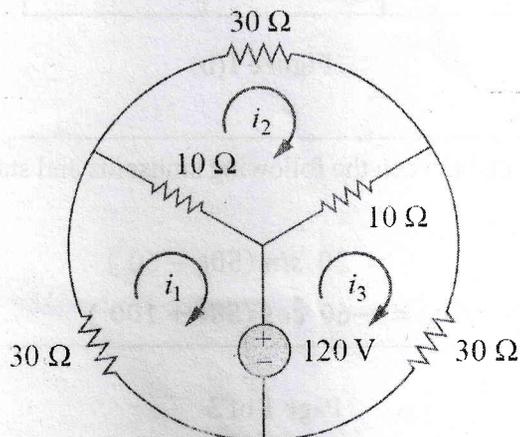


Figure 3(b)

4. a) Evaluate the condition for maximum power transfer in a DC circuit. [04]

b) Solve for v_1 , v_2 and v_3 in the circuit of figure 4(b) using Nodal analysis. [06]

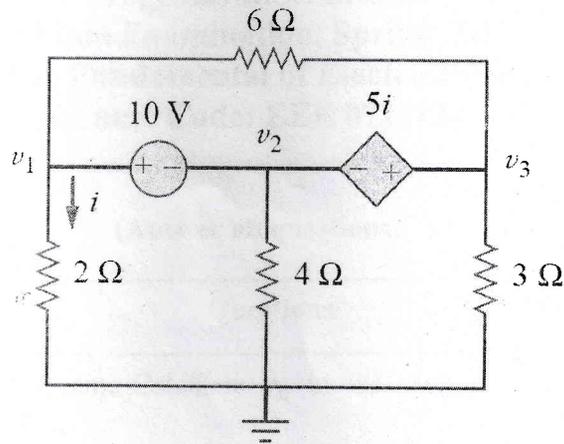


Figure 4(b)

5. a) Calculate I_o in the circuit of figure 5(a) applying Nodal analysis. [05]

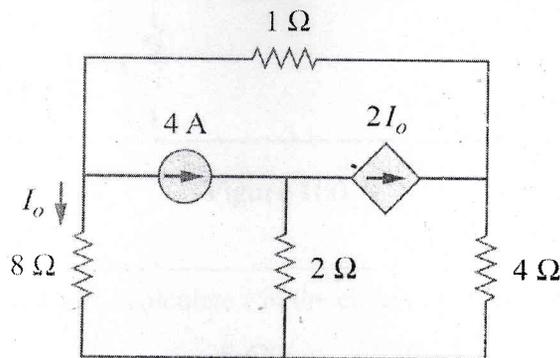


Figure 5(a)

b) Calculate the value of $i_s(t)$ in the circuit of figure 5(b). [05]

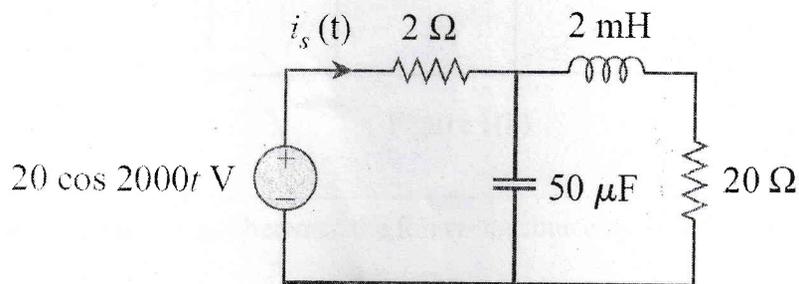


Figure 5(b)

University of Information Technology & Sciences (UITS)

Faculty of Science and Engineering

Department of Computer Science and Engineering

Program: B.Sc. in CSE

Term Final Examination, Spring 2025

Course Title: Fundamental of Electrical Engineering

Course Code: EEE 0713121

Marks: 50

Time: 3(Three) hours

(Answer all questions)

Q. No.	Questions	Marks
1.	<p>a) State Superposition theorem. Calculate v_o in the circuit of figure 1(a) applying Superposition principle.</p> <div style="text-align: center;"> </div> <p style="text-align: center;">Figure 1(a)</p> <p style="text-align: right; font-style: italic;">8.689 4.347 6.75 -0.608</p>	[05]
b)	<p>Use Source Transformation to calculate i in the circuit of figure 1(b).</p> <div style="text-align: center;"> </div> <p style="text-align: center;">Figure 1(b)</p>	[05]
2.	<p>a) Compute the phase angle between the following sinusoids and state which one lags the other.</p> $v_1 = 20 \sin(50t + 60^\circ)$ $v_2 = -60 \cos(50t + 100^\circ)$	[04]

- b) State Thevenin's theorem. Apply Thevenin's theorem to compute V_o in the circuit of figure 2(b). [06]

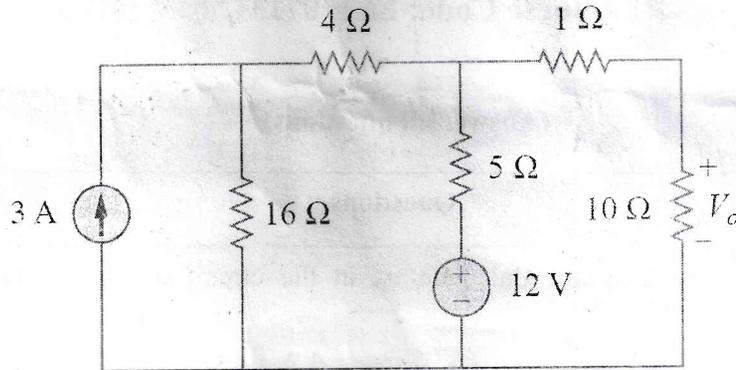


Figure 2(b)

3. a) Analyze and illustrate the Norton equivalent circuit with respect to terminals a-b in the circuit shown in figure 3(a). [05]

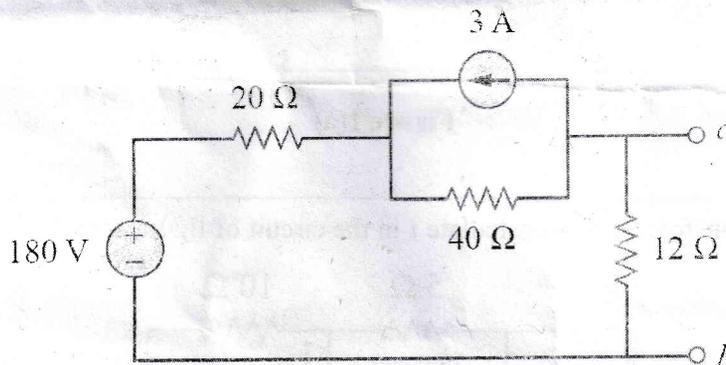


Figure 3(a)

- b) Solve for i_1 , i_2 and i_3 in the circuit of figure 3(b) using Mesh analysis. [05]

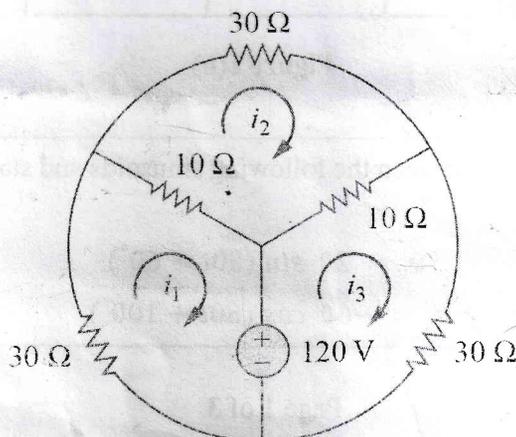


Figure 3(b)

303

4. a) Evaluate the condition for maximum power transfer in a DC circuit. [04]

b) Solve for v_1 , v_2 and v_3 in the circuit of figure 4(b) using Nodal analysis. [06]

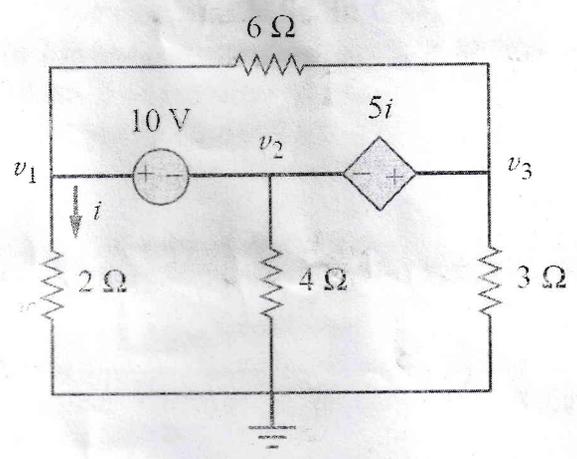


Figure 4(b)

Handwritten calculations for Figure 4(b):

$$\begin{array}{r} -2.2 \\ -8.8 \\ \hline 21.4 \\ \hline 1.2 \end{array}$$

$$\begin{array}{r} 37.2, 6 \\ \hline 1.2, 2 \end{array}$$

5. a) Calculate I_0 in the circuit of figure 5(a) applying Nodal analysis. [05]

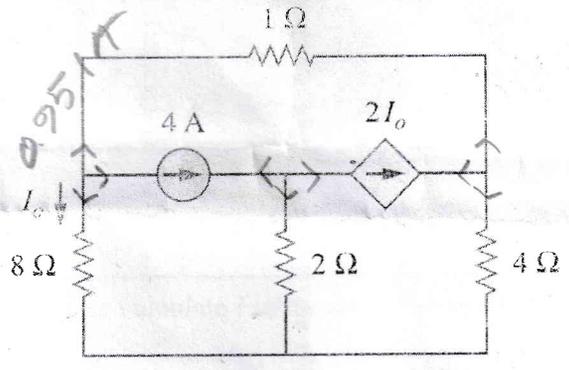


Figure 5(a)

Handwritten calculations for Figure 5(a):

$$\begin{array}{r} 0.95 \\ \hline 21.4 \\ \hline 1.2 \end{array}$$

$$\begin{array}{r} -7.67 \\ 11.80 \\ \hline -4.57 \end{array}$$

$$\begin{array}{r} 33.6 \\ \hline 1.2 \end{array}$$

b) Calculate the value of $i_s(t)$ in the circuit of figure 5(b). [05]

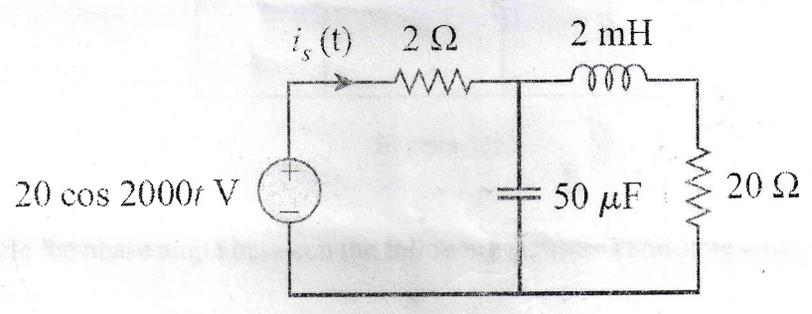


Figure 5(b)