

5.7 Amey

University of Information Technology & Sciences (UITS)
Faculty of Science and Engineering
Department of Computer Science and Engineering
Program: B.Sc. in CSE
Term Final Examination, Autumn 2025
Course Title: Fundamental of Electrical Engineering
Course Code: EEE 0713121

Marks: 50

Time: 3 (Three) hours

(Answer all questions)

- | Q. No. | Questions | Marks |
|--------|---|-------|
| 1. | a) Find the voltages at the three non-reference nodes in the circuit of figure 1(a) using Nodal analysis. | [06] |

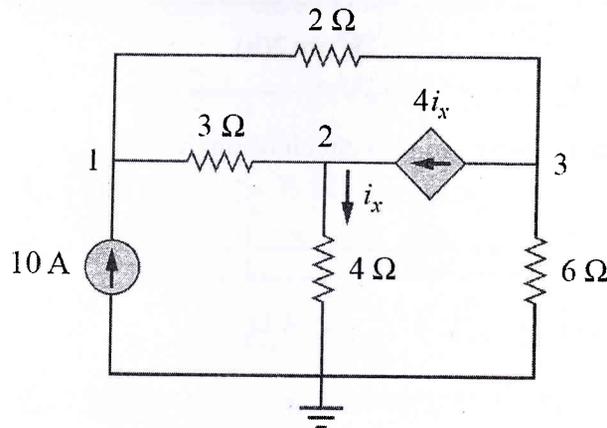


Figure 1(a)

- | | | |
|----|--|------|
| | b) Evaluate the condition for maximum power transfer in a DC circuit. | [04] |
| 2. | a) Apply mesh analysis to calculate i in the circuit of figure 2(a). | [04] |

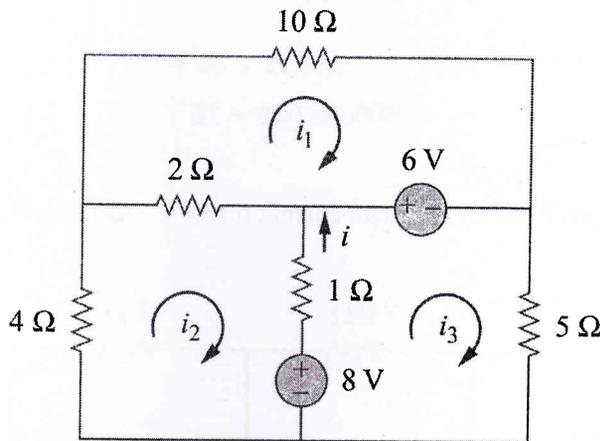


Figure 2(a)



- b) State Superposition Theorem. Determine v_0 in the circuit of figure 2(b) using the Superposition principle. [06]

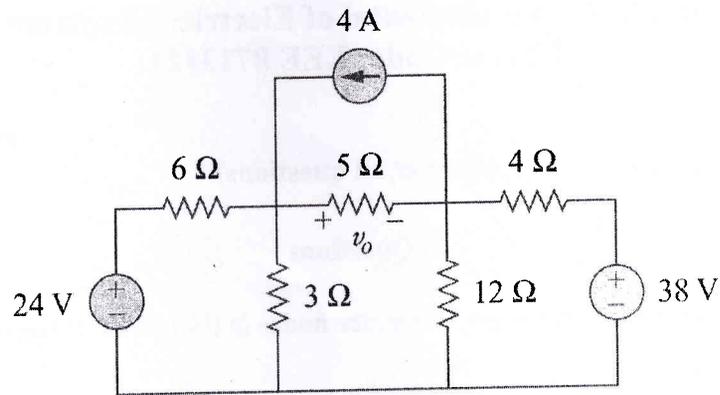


Figure 2(b)

3. a) Use mesh analysis to obtain i_0 in the circuit of figure 3(a). [06]


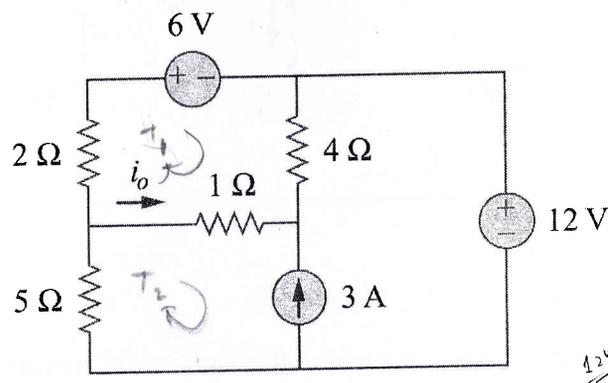


Figure 3(a)

- b) Compute the phase angle between the following sinusoids and state which one lags the other. [04]

$$v_1 = 20 \sin (wt + 60^\circ)$$

$$v_2 = 60 \cos (wt - 10^\circ)$$

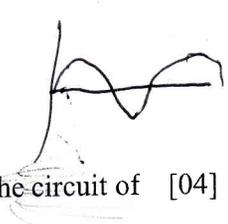

4. a) Use Source Transformation to calculate current through 8 Ω resistor in the circuit of figure 4(a). [04]

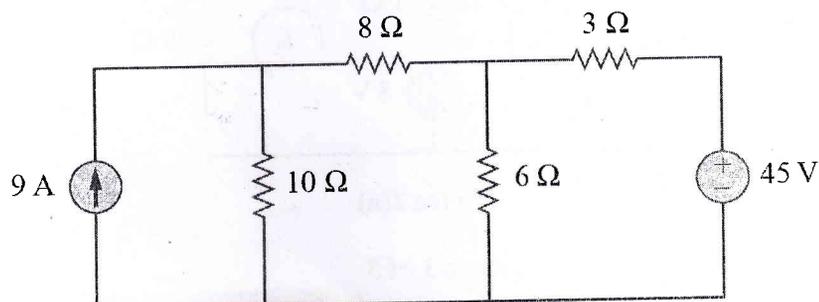


Figure 4(a)



- b) State Thevenin's Theorem. Apply Thevenin's theorem to find V_0 in the circuit of figure 4(b). [06]

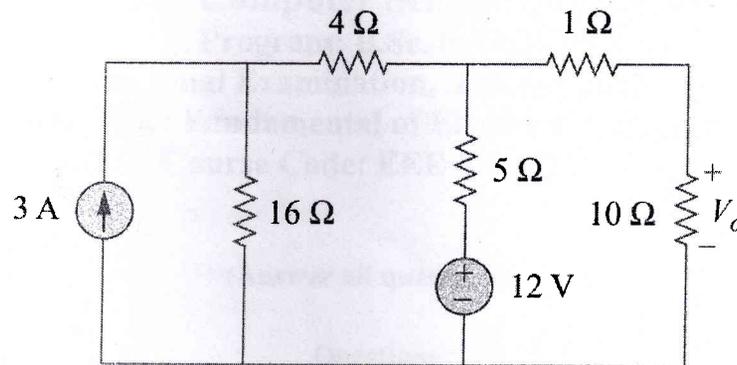


Figure 4(b)

5. a) Determine the Norton equivalent at the terminals a-b of the circuit in figure 5(a). [05]

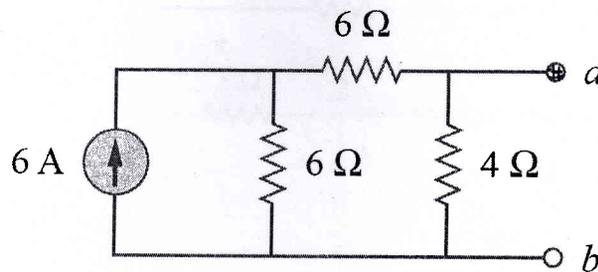


Figure 5(a)

- b) Let $i_s(t) = 5 \cos(100t + 40^\circ)$ A. Solve for v_x in the circuit of figure 5(b). [05]

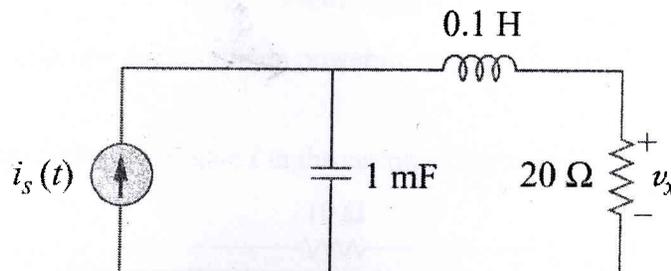


Figure 5(b)

